



# Pipelining and Parallel Processing


Shao-Yi Chien

# Introduction


- Pipelining and parallel are the most important design techniques in VLSI DSP systems
- Make use of the inherent parallel property of DSP algorithms
  - Pipelining: different function units working in parallel
  - Parallel: duplicated function units working in parallel

Parallel processing and pipelining techniques are duals of each other.  
If a computation can be pipelined, it can also be processed in parallel.


# An Example: Car Production Line

 

 Cost: 1      10 cars/month  
Throughput:  $1/mT$   
Latency:  $mT$       3 days



 Cost:  $>1$   
Throughput:  $1/T$       30 cars/month  
Latency:  $>mT$       ~ 3 day  
                    (slightly  $> mT$ )




Cost:  $>n$        $>3$   
Throughput:  $(1/mT)*n$       10 cars/month  $\times 3 = 30$  cars/month  
Latency:  $>mT$       3 days

**Throughput:** how many cars produced in one hour  
**Latency:** how long will it take to produce one car

# Pipelining of Digital Filters (1/3)

## ■ FIR filter

$$y(n) = ax(n) + bx(n-1) + cx(n-2).$$

 


□ Critical path:  $T_M + 2T_A$

$$T_{sample} \geq T_M + 2T_A \quad f_{sample} \leq \frac{1}{T_M + 2T_A}$$

"f" pipeline

# Pipelining of Digital Filters (2/3)


## ■ Pipelined FIR filter

 

$$T_{sample} \geq T_M + T_A \quad f_{sample} \leq \frac{1}{T_M + T_A}$$

# Pipelining of Digital Filters (3/3)

## ■ Schedule

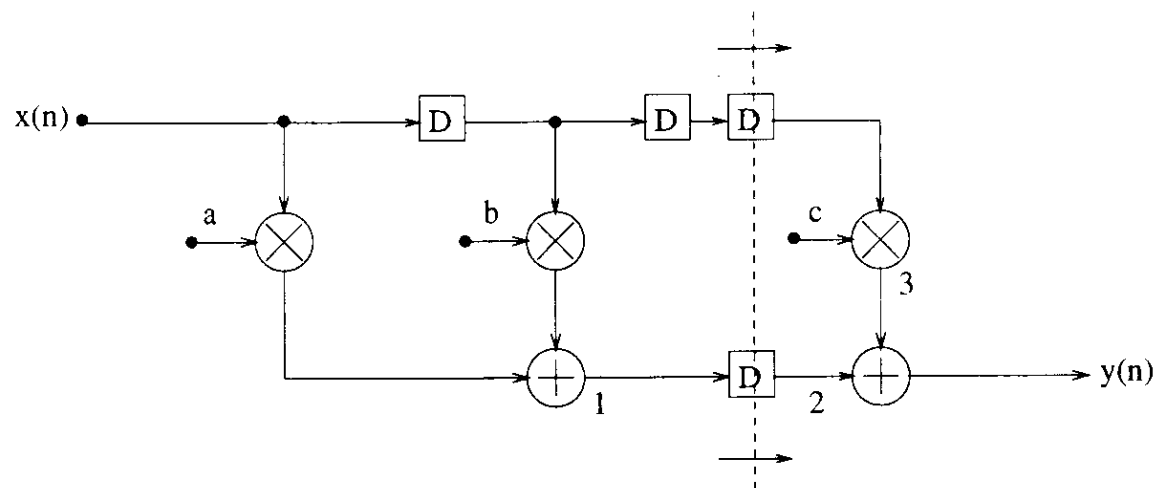

Clock	Input	Node 1	Node 2	Node 3	Output
0	$x(0)$	$ax(0) + bx(-1)$	—	—	—
1	$x(1)$	$ax(1) + bx(0)$	$ax(0) + bx(-1)$	$cx(-2)$	$y(0)$
2	$x(2)$	$ax(2) + bx(1)$	$ax(1) + bx(0)$	$cx(-1)$	$y(1)$
3	$x(3)$	$ax(3) + bx(2)$	$ax(2) + bx(1)$	$cx(0)$	$y(2)$

# Pipeline

- Can reduce the critical path to increase the working frequency and sample rate

- $T_M + 2T_A \rightarrow T_M + T_A$

# Drawbacks of Pipelining

- Increasing latency (in cycle) *for a 2-level pipelined system,  $\Rightarrow$  1-cycle latency*

- For M-level pipelined system, the number of delay elements in any path from input to output is (M-1) greater than the origin one

- Increase the number of latches (registers)

*Cut 1D data  $\Rightarrow$  Register(s)*

*Cut 2D data  $\Rightarrow$  line buffer(s)*




*Cut 3D data  $\Rightarrow$  frame buffer(s)*

*depends on where you cut*



   
# How to Do Pipelining?

- Put pipelining latches across any **feed-forward cutset** of the graph
- Cutset "bridges"
  - A cutset is a set of edges of a graph such that if these edges are removed from the graph, the graph becomes disjoint
- Feed-forward cutset
  - The data move in the forward direction on all the edges of the cutset





# How to Do Pipelining?

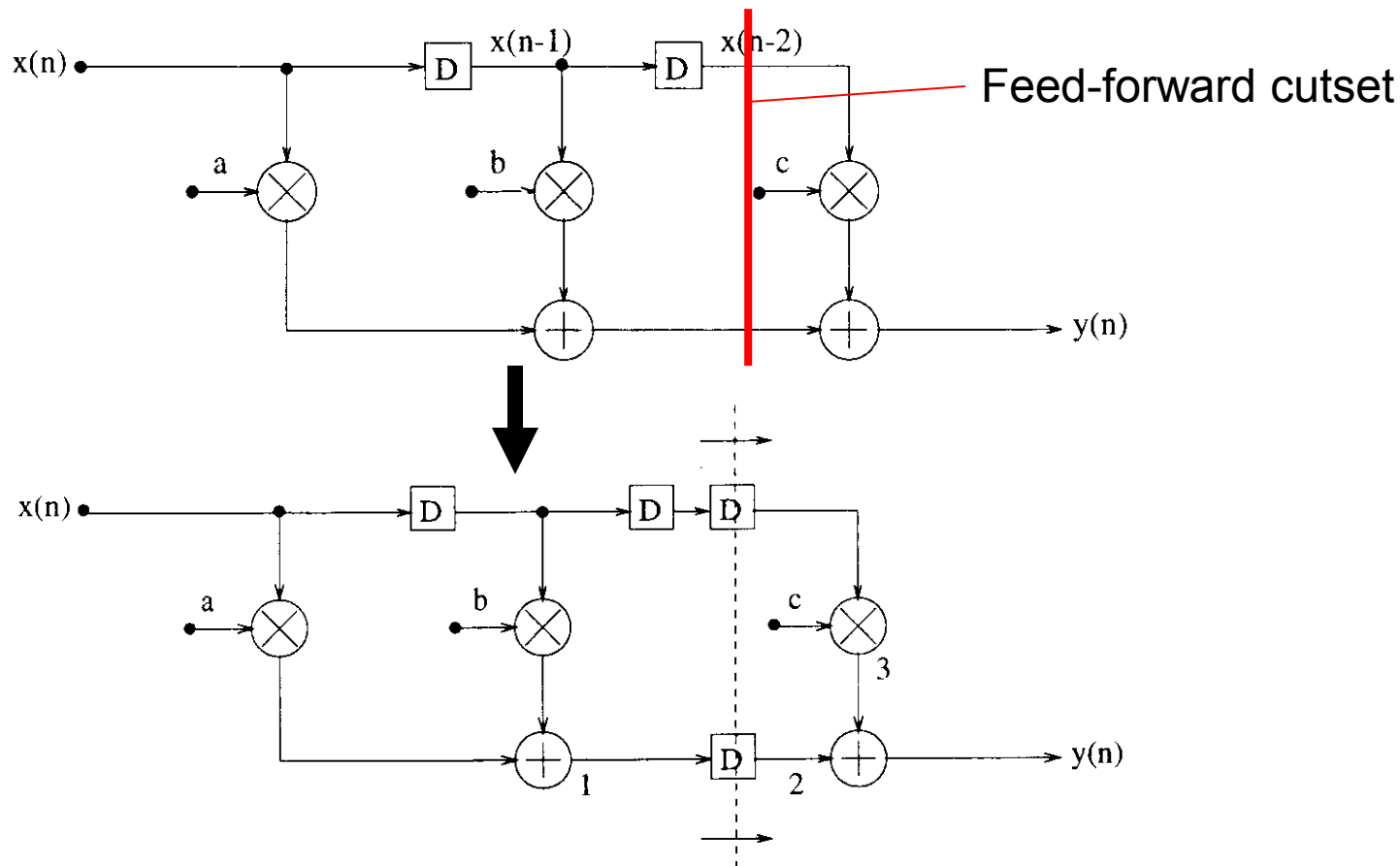

 
 
# Example

- In the SFG in Fig. (a), all the computation time for each node is 1 u.t.
- (a) Calculate the critical path
- (b) The critical path is reduced to 2 u.t. by inserting 3 extra delay elements. Is it a valid pipelining?



# Fine-Grain Pipelining

e.g. Array Multiplier

  

## ■ Critical path ( $T_M=10$ , $T_A=2$ )

- $T_M + 2T_A = 14$
- $T_M + T_A = 12$
- $T_{M1} = 6$  or  $T_{M2} + T_A = 6$

# Notes for Pipelining (1/2)

- Pipelining is a very simple design technique which can maintain the input output data configuration and sampling frequency

- $T_{\text{clk}} = T_{\text{sample}}$

- Supported in many EDA tools

Modern EDA tools support automatic low-level pipelining. However, system level pipelining still heavily rely on designers. e.g.) Designware pipelined multiplier.

- Still has some limitations

- ☐ Pipeline bubbles *conditional / flushes ↓ efficiency*
- ☐ Has some problems for recursive system *(has feedback loop)*
- ☐ Introduces large hardware cost for 2-D or 3-D data
- ☐ Communication bound *Although pipelined design ↑ speed, Data I/O couldn't keep up*



# Notes for Pipelining (2/2)

## ■ Effective pipelining

- Put pipelining registers on the critical path

- Balance pipelining

- $10 \rightarrow (2+8)$ : critical path=8

- $10 \rightarrow (5+5)$ : critical path=5

# Parallel of Digital Filters (1/5)

- Single-input single-output (SISO) system


$$y(n) = ax(n) + bx(n-1) + cx(n-2).$$

- Multiple-input multiple-output (MIMO) system

$$y(3k) = ax(3k) + bx(3k-1) + cx(3k-2)$$

$$y(3k+1) = ax(3k+1) + bx(3k) + cx(3k-1) \quad \text{3-Parallel System!}$$
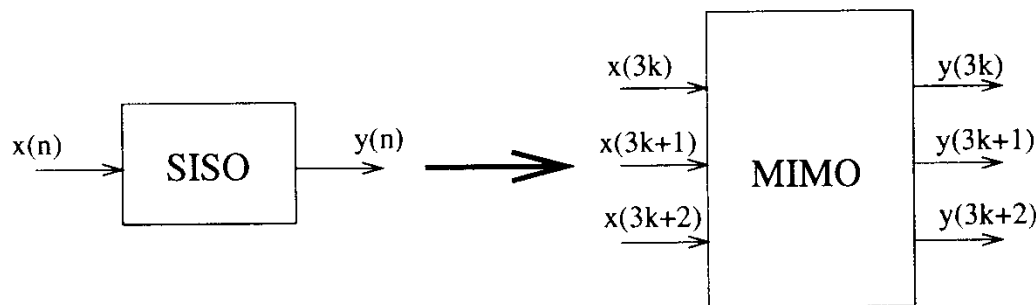
$$y(3k+2) = ax(3k+2) + bx(3k+1) + cx(3k).$$



Sequential System


3-Parallel System

# Parallel of Digital Filters (2/5)

- Parallel processing, block processing
- Block size ( $L$ ): the number of data to be processed at the same time
- Block delay ( $L$ -slow)
  - A latch is equivalent to  $L$  clock cycles at the sample rate



# Parallel of Digital Filters (3/5)

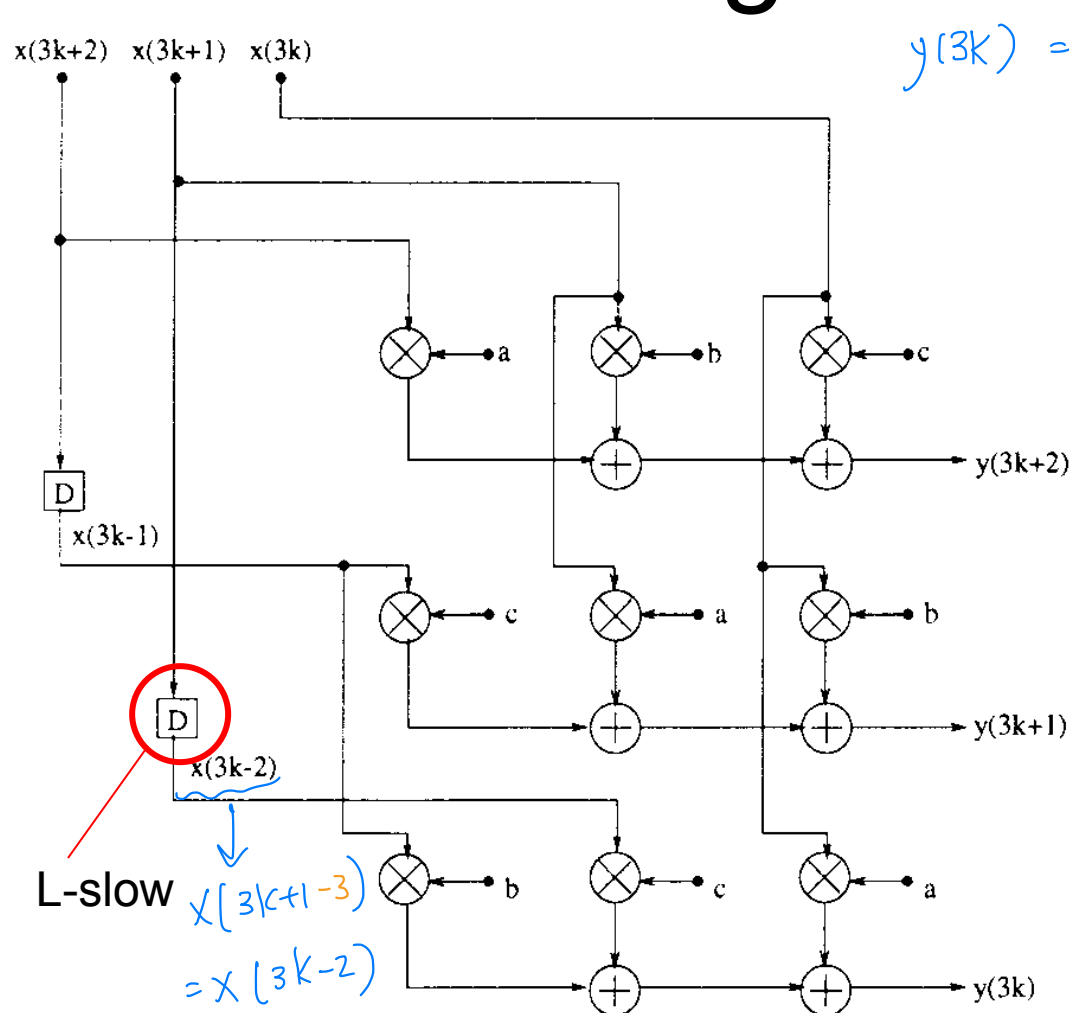

$$y(3k) = ax(3k) + bx(3k-1) + cx(3k-2)$$

$$T_{clk} \geq T_M + 2T_A$$

The critical path is the same

$$T_{iter} = T_{sample} = \frac{1}{L} T_{clk} \geq \frac{1}{3} (T_M + 2T_A)$$


$T_{clk}$  is not equal to  $T_{sample}$

now each  $T_{clk}$  could process 3 data.


$T_{sample}$  could be reduce to  $\frac{1}{3} T_{sample}$

# Parallel of Digital Filters (4/5)


## ■ Whole system

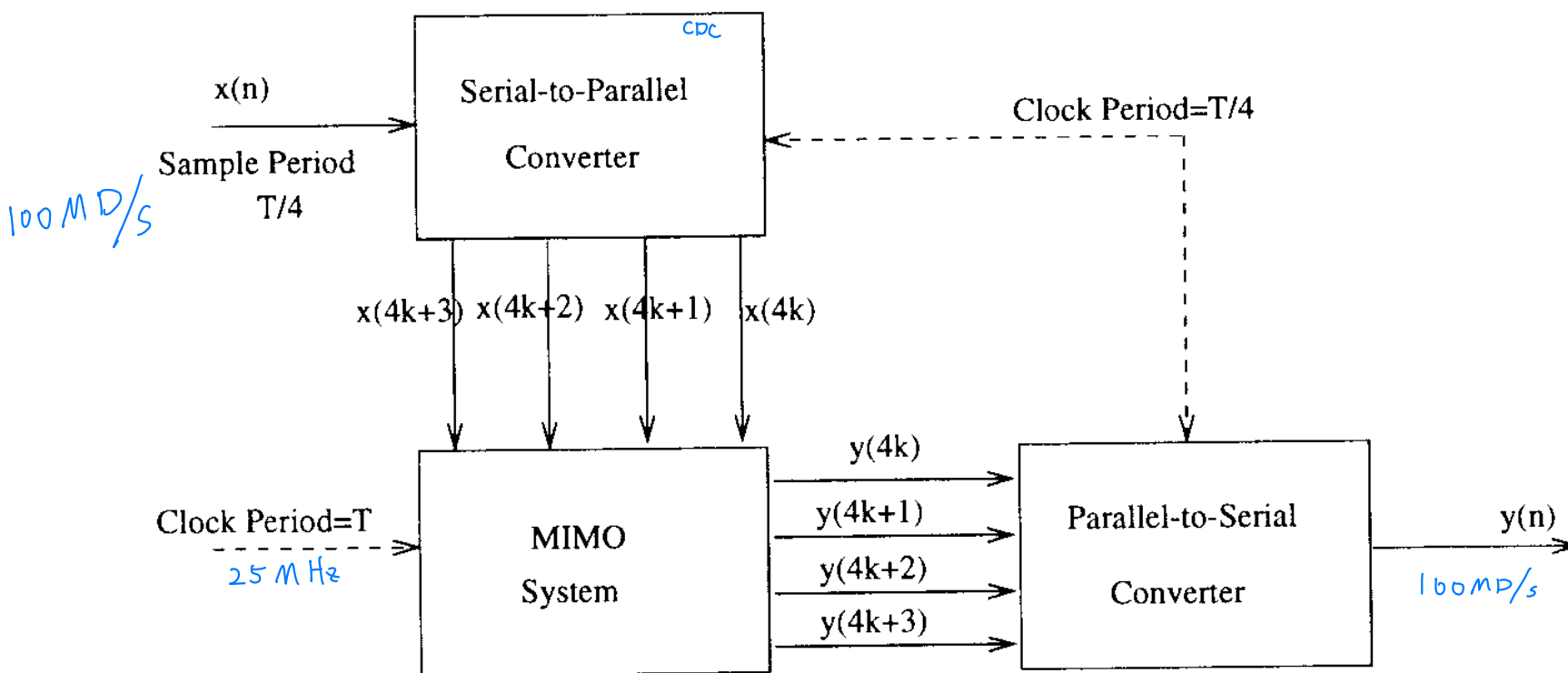

# Parallel of Digital Filters (5/5)

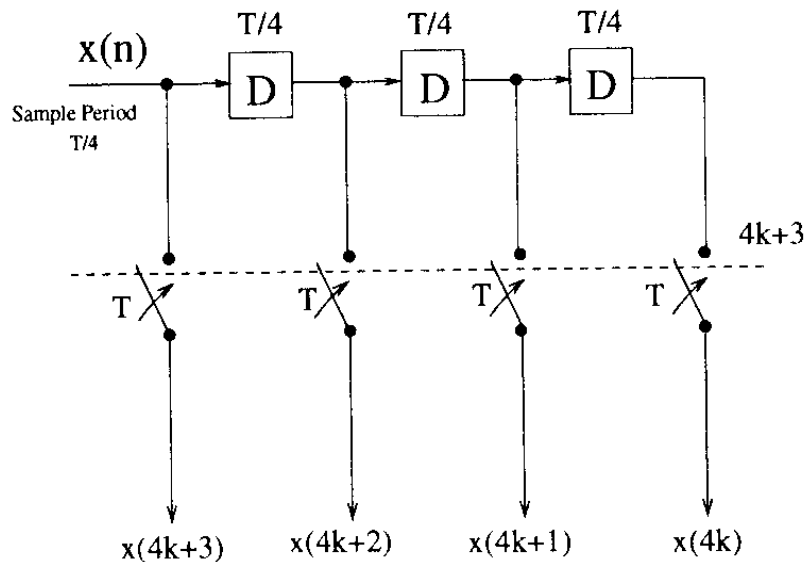


Serial-to-parallel converter

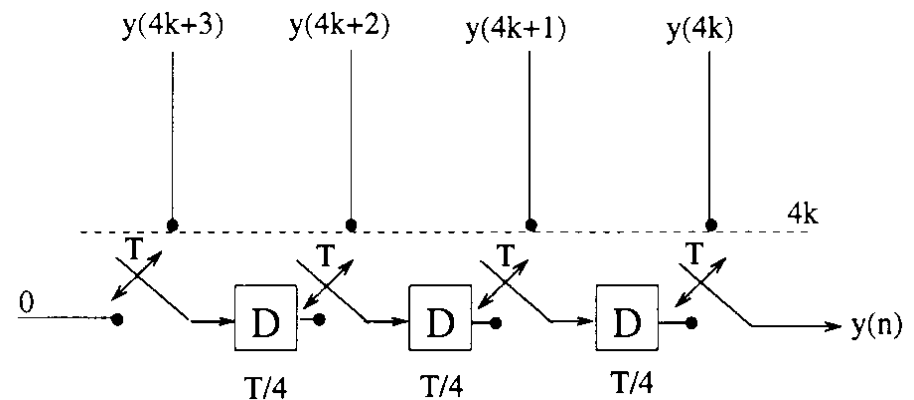

Parallel-to-serial converter
 
# Parallel Processing v.s. Pipelining


- Parallel processing is superior than pipelining processing for the I/O bottleneck (communication bounded)
  - Pipelining only can increase the clock rate
  - System clock rate = sample rate for pipelining system
  - Use parallel processing can further lower the required working frequency



# Pipelining-Parallel Architecture

$x(3k+2)$   $x(3k+1)$   $x(3k)$

*Mind feedforward CntSet.*

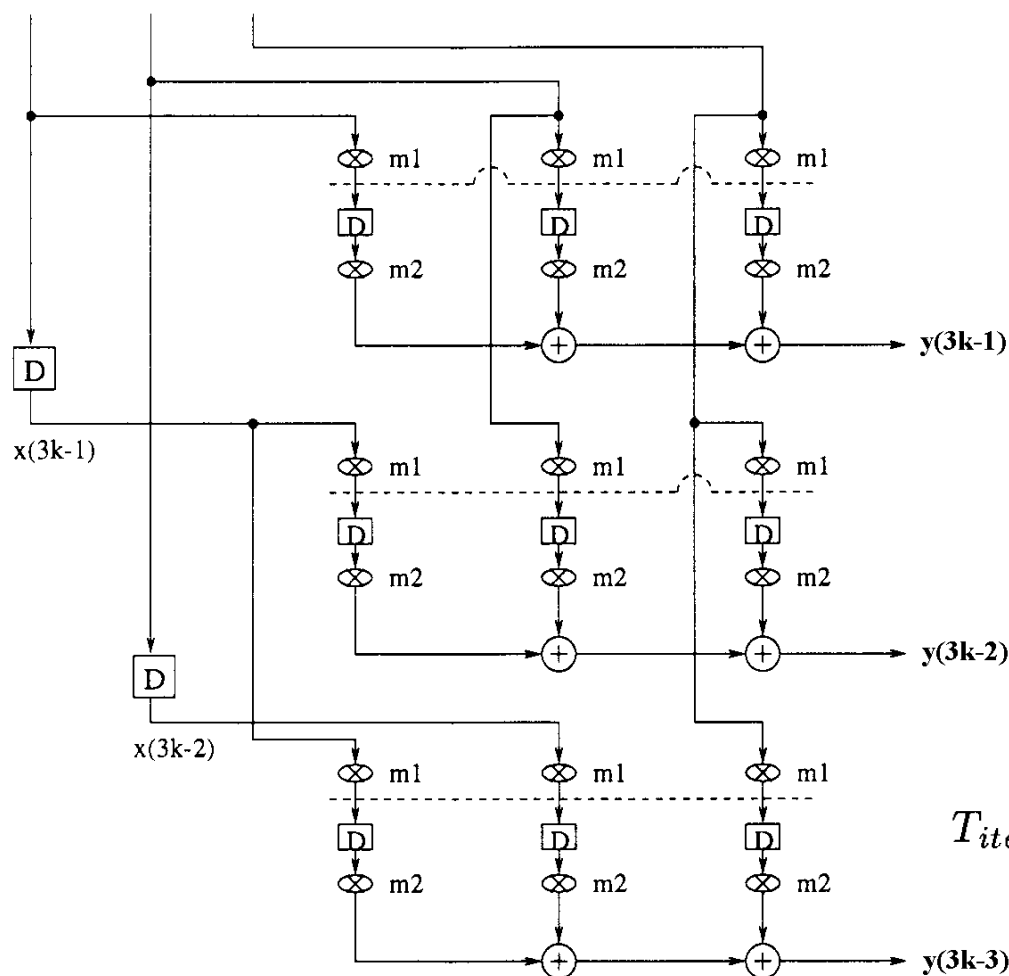


$$T_{iter} = T_{sample} = \frac{1}{LM} T_{clk} = \frac{1}{6} (T_M + 2T_A)$$

# Notes for Parallel Processing

- The input/output data access scheme should be carefully designed, it will cost a lot sometimes
- $T_{\text{clk}} > T_{\text{sample}}$ ,  $f_{\text{clk}} < f_{\text{sample}}$
- Large hardware cost
- Combined with pipelining processing

# Low Power Issues

 

Overdesign,  $V \downarrow$   
 How to design a 2 GHz low-power CPU? Design a 3 GHz CPU & run it at 2 GHz by  $V \downarrow$

- Pipelining and parallel processing are also beneficial for low power design  $\sum \text{Critical Path Capacitance}$

- Propagation delay

$$T_{pd} = \frac{C_{charge} V_0}{k(V_0 - V_t)^2}$$

- Power consumption

$= \alpha \cdot C \cdot V^2 \cdot f$ ,  $\alpha$ : toggle rate

dynamic power:  $P = C_{total} V_0^2 f$   $f = \frac{1}{T_{seq}}$


static power (leakage)  $\propto A \cdot V_0$

- Assume the sampling frequency is the same

# Pipelining for Low Power (1/2)
 
## ■ For M-level pipelining

- Critical path is reduced to  $1/M$
- The capacitance is also reduced to  $C_{\text{charge}}/M$
- The supply voltage can be reduced to  $\beta V_0$ , and the sampling period remains unchanged





# Pipelining for Low Power (2/2)

- Power consumption:

$$P_{pip} = C_{total} \beta^2 V_0^2 f = \beta^2 P_{seq}$$

- How about the parameter  $\beta$  ?

$$T_{seq} = \frac{C_{charge} V_0}{k(V_0 - V_t)^2}$$

||

$$T_{pip} = \frac{\frac{C_{charge}}{M} \beta V_0}{k(\beta V_0 - V_t)^2}$$

$$\longrightarrow M(\beta V_0 - V_t)^2 = \beta(V_0 - V_t)^2$$

Solve this equation to get  $\beta$

# Example

$$\frac{(C_M + C_A) \cdot V}{K(V - V_t)^2} = \frac{6 C_A \cdot V}{K(V - V_t)^2}$$



$$\frac{(C_M + C_A) \cdot V_0}{K(V_0 - V_t)^2}$$

## Parameters

- ☐  $T_M = 10$  u.t.
- ☐  $T_A = 2$  u.t.
- ☐  $T_{m1} = 6$  u.t.
- ☐  $T_{m2} = 4$  u.t.
- ☐  $C_M = 5C_A$
- ☐  $V_t = 0.6V$  *threshold voltage*
- ☐ Normal  $V_{cc} = 5V$

■ (a) New supply voltage?

■ (b) Power saving percentage?

 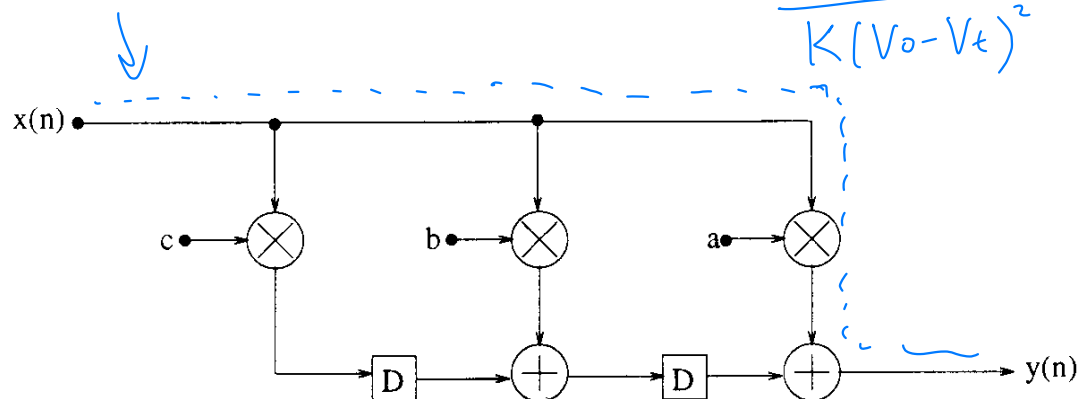

# Answer

(a)

Origin system:  $C_{charge} = C_M + C_A = 6C_A$

Pipelined system:  $C_{charge} = C_{m1} = C_{m2} + C_A = 3C_A$

$$\longrightarrow 50\beta^2 - 31.36\beta + 0.72 = 0$$

$$\beta = 0.6033, \text{ or } \beta = 0.0239$$

Invalid value, less than threshold voltage

$$V_{pip} = \beta V_0 = 3.0165 \text{ V.}$$

(b)


$$Ratio = \beta^2 = 36.4\%.$$



# Parallel Processing for Low Power (1/2)
 
## ■ For L-parallel system

- Clock period:  $T_{seq} \rightarrow LT_{seq}$
- $C_{charge}$  remains unchanged
- $C_{total} \rightarrow LC_{total}$
- Have more time to charge the capacitance, the supply voltage can be lower  $\beta V_0$



# Parallel Processing for Low Power (2/2)

## ■ Power consumption

$$\begin{aligned}P_{par} &= (LC_{total})(\beta V_0)^2 \frac{f}{L} \\&= \beta^2 C_{total} V_0^2 f \\&= \beta^2 P_{seq}\end{aligned}$$

## ■ To derive the parameter $\beta$

$$\begin{aligned}T_{seq} &= \frac{C_{charge} V_0}{k(V_0 - V_t)^2} \\ \downarrow \\ LT_{seq} &= \frac{C_{charge} \beta V_0}{k(\beta V_0 - V_t)^2} \longrightarrow L(\beta V_0 - V_t)^2 = \beta(V_0 - V_t)^2\end{aligned}$$

Not always equal


# Example

## Parameters

- $T_M = 8$  u.t.
- $T_A = 1$  u.t.
- $T_{\text{sample}} = 9$  u.t.
- $C_M = 8C_A$
- $V_t = 0.45V$
- Normal  $V_{cc} = 3.3V$

■ (a) New supply voltage?

■ (b) Power saving percentage?

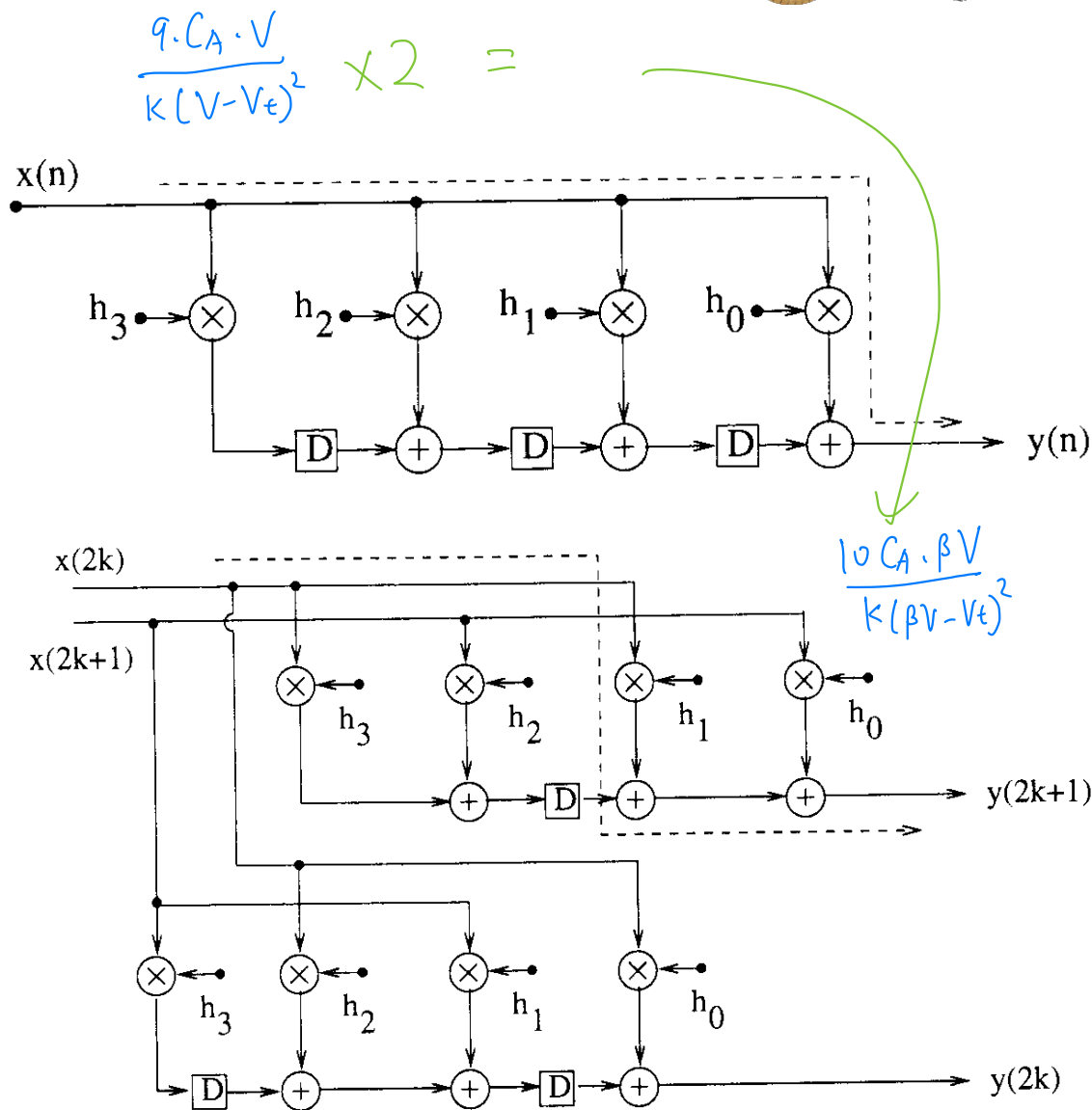

# Answer

(a)

Origin:  $C_{charge} = C_M + C_A = 9C_A$

2-parallel system:  $C_{charge} = C_M + 2C_A = 10C_A$

$$T_{seq} = \frac{9C_A V_0}{k(V_0 - V_t)^2},$$

$$5\beta(V_0 - V_t)^2 = 9(\beta V_0 - V_t)^2$$

$$T_{par} = \frac{10C_A \beta V_0}{k(\beta V_0 - V_t)^2}.$$

$$\beta = 0.6589, \text{ or } \beta = 0.0282.$$


Invalid value, less than threshold voltage

(b)

$$Ratio = \beta^2 = 43.41\%.$$



# Pipelining-Parallel for Low Power

 

$$LT_{pd} = \frac{(C_{charge}/M)\beta V_o}{k(\beta V_o - V_t)^2} = \frac{LC_{charge}V_o}{k(V_o - V_t)^2}.$$

$$ML(\beta V_o - V_t)^2 = \beta(V_o - V_t)^2$$



# Conclusion

## ■ Pipelining

- ☐ Reduce the critical path
- ☐ Increase the clock speed
- ☐ Reduce power consumption at the same speed

## ■ Parallel

- ☐ Increase effective sampling rate
- ☐ Reduce power consumption at the same speed