




Folding

Shao-Yi Chien

Introduction

- Folding transform is used to systematically determine the control circuits in DSP architectures where multiple algorithm operations are **time-multiplexed** to a single functional unit
 - Trading area for time in a DSP architecture
 - Reducing the number of hardware functional units by a factor of N at the expense of increasing the computation time by a factor of N

An Example of Folding

 


Scheduling

Cycle	Adder Input (left)	Adder Input (top)	System Output
0	$a(0)$	$b(0)$	—
1	$a(0) + b(0)$	$c(0)$	—
2	$a(1)$	$b(1)$	$a(0) + b(0) + c(0)$
3	$a(1) + b(1)$	$c(1)$	—
4	$a(2)$	$b(2)$	$a(1) + b(1) + c(1)$
5	$a(2) + b(2)$	$c(2)$	—



Folding Transform

 N : folding factor
 u, v are namely folding orders
 $0 \leq u, v \leq N-1$
 H_U H_V
 $@Nl+u$ $@Nl+v$



$$D_F(U \xrightarrow{e} V) = [N(l + w(e)) + v] - [Nl + P_U + u] = Nw(e) - P_U + v - u$$

- (1) U is executed in H_U and V is executed in H_V
- (2) Data leave H_U at $Nl + \underline{u}$, and reach H_V at $Nl + \underline{v}$
- (3) H_U is pipelined by P_U stages



Folding Transform

■ Folding set

- Ex: a folding set $S_1 = \{A_1, \phi, A_2\}$ for $N=3$ for a functional unit means A_1 is executed at time $3l+0$ ($S_1|0$), and A_2 is executed at time $3l+2$ ($S_1|2$)



Folding Transform

$$N = |S_1| = |S_2| = 4$$


$w(e)$: delay on the path

P_U : Pipeline stages

v : Dest. node index e.g. $(S_1|1) = 1$

u : Source node index
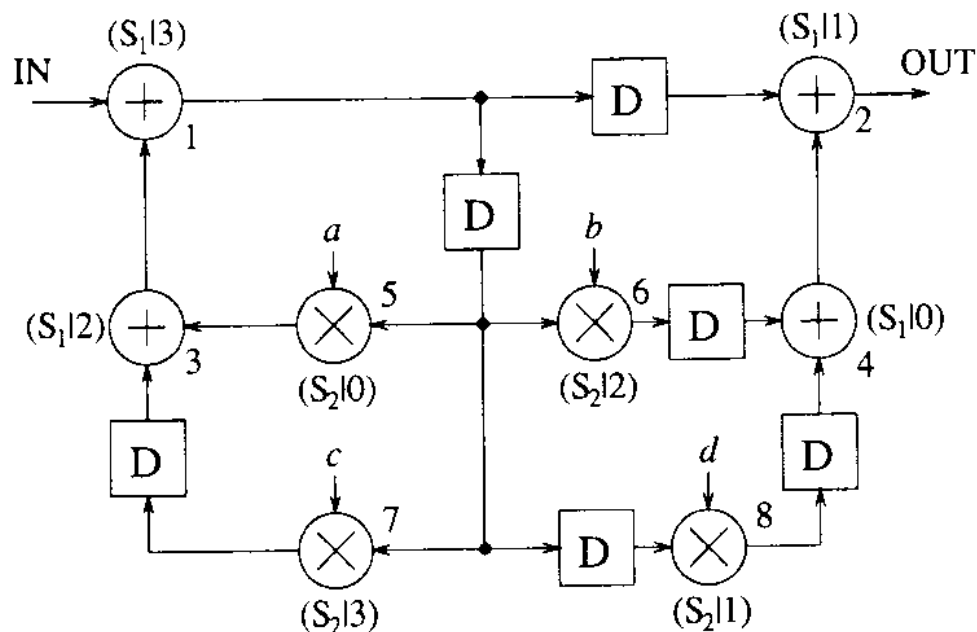
$$D_F(U \xrightarrow{e} V) = [N(l + w(e)) + v] - [Nl + P_U + u] = Nw(e) - P_U + v - u$$




$$\begin{aligned} D_F(1 \rightarrow 2) &= 4(1) - 1 + 1 - 3 = 1 \\ D_F(1 \rightarrow 5) &= 4(1) - 1 + 0 - 3 = 0 \\ D_F(1 \rightarrow 6) &= 4(1) - 1 + 2 - 3 = 2 \\ D_F(1 \rightarrow 7) &= 4(1) - 1 + 3 - 3 = 3 \\ D_F(1 \rightarrow 8) &= 4(2) - 1 + 1 - 3 = 5 \\ D_F(3 \rightarrow 1) &= 4(0) - 1 + 3 - 2 = 0 \\ D_F(4 \rightarrow 2) &= 4(0) - 1 + 1 - 0 = 0 \\ D_F(5 \rightarrow 3) &= 4(0) - 2 + 2 - 0 = 0 \\ D_F(6 \rightarrow 4) &= 4(1) - 2 + 0 - 2 = 0 \\ D_F(7 \rightarrow 3) &= 4(1) - 2 + 2 - 3 = 1 \\ D_F(8 \rightarrow 4) &= 4(1) - 2 + 0 - 1 = 1. \end{aligned}$$


$S_1 = \{4, 2, 3, 1\}$ for one adder with 1 stage pipelining $P_A = 1$


$S_2 = \{5, 8, 6, 7\}$ for one multiplier with 2 stages pipelining $P_M = 2$

$N = 4$

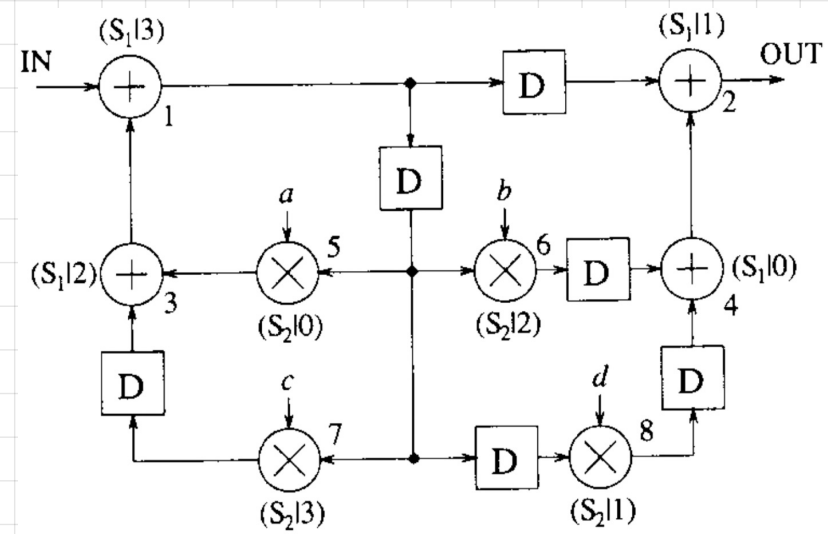


$$\begin{aligned}
 D_F(1 \rightarrow 2) &= 4(1) - 1 + 1 - 3 = 1 \\
 D_F(1 \rightarrow 5) &= 4(1) - 1 + 0 - 3 = 0 \\
 D_F(1 \rightarrow 6) &= 4(1) - 1 + 2 - 3 = 2 \\
 D_F(1 \rightarrow 7) &= 4(1) - 1 + 3 - 3 = 3 \\
 D_F(1 \rightarrow 8) &= 4(2) - 1 + 1 - 3 = 5 \\
 D_F(3 \rightarrow 1) &= 4(0) - 1 + 3 - 2 = 0 \\
 D_F(4 \rightarrow 2) &= 4(0) - 1 + 1 - 0 = 0 \\
 D_F(5 \rightarrow 3) &= 4(0) - 2 + 2 - 0 = 0 \\
 D_F(6 \rightarrow 4) &= 4(1) - 2 + 0 - 2 = 0 \\
 D_F(7 \rightarrow 3) &= 4(1) - 2 + 2 - 3 = 1 \\
 D_F(8 \rightarrow 4) &= 4(1) - 2 + 0 - 1 = 1.
 \end{aligned}$$

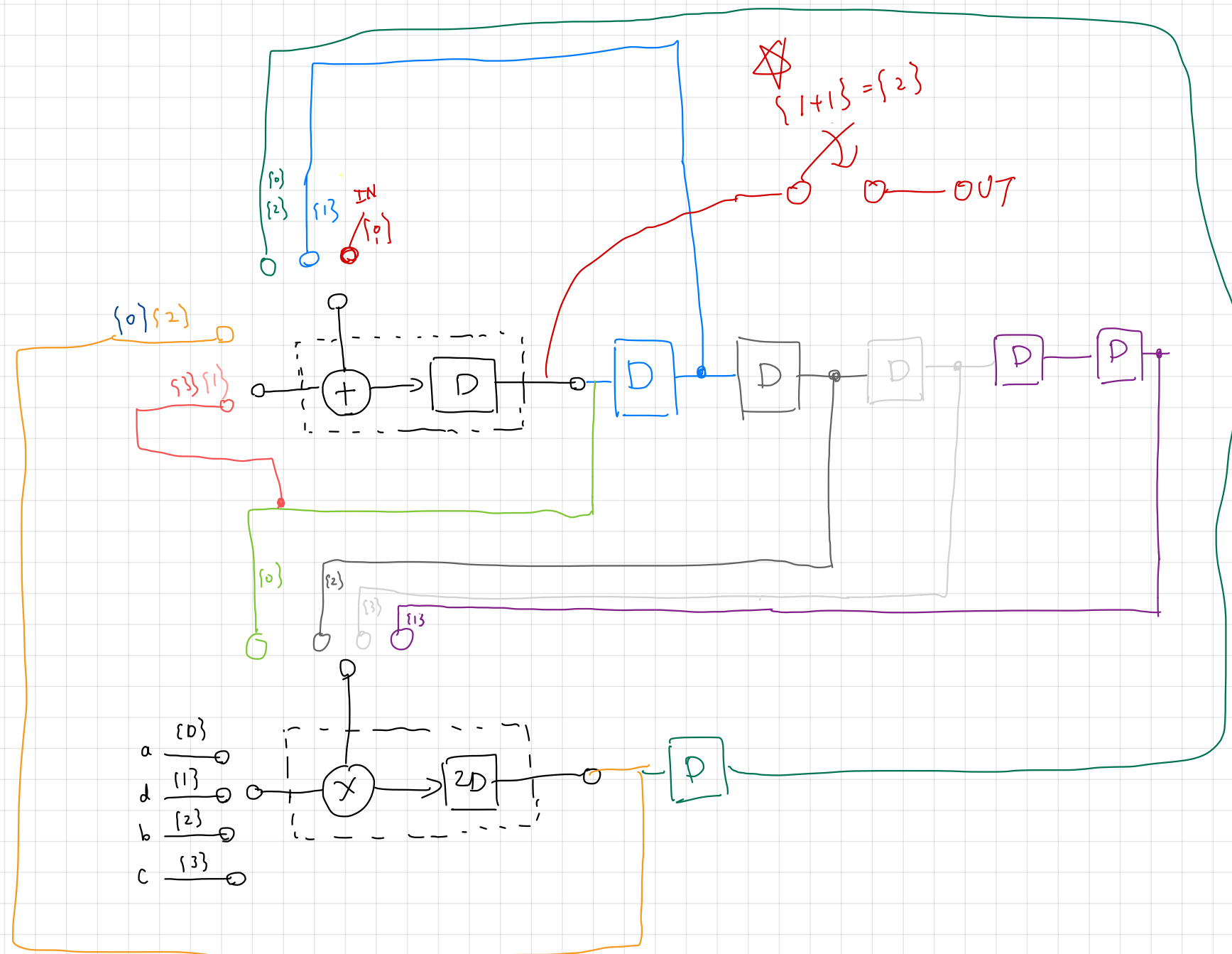

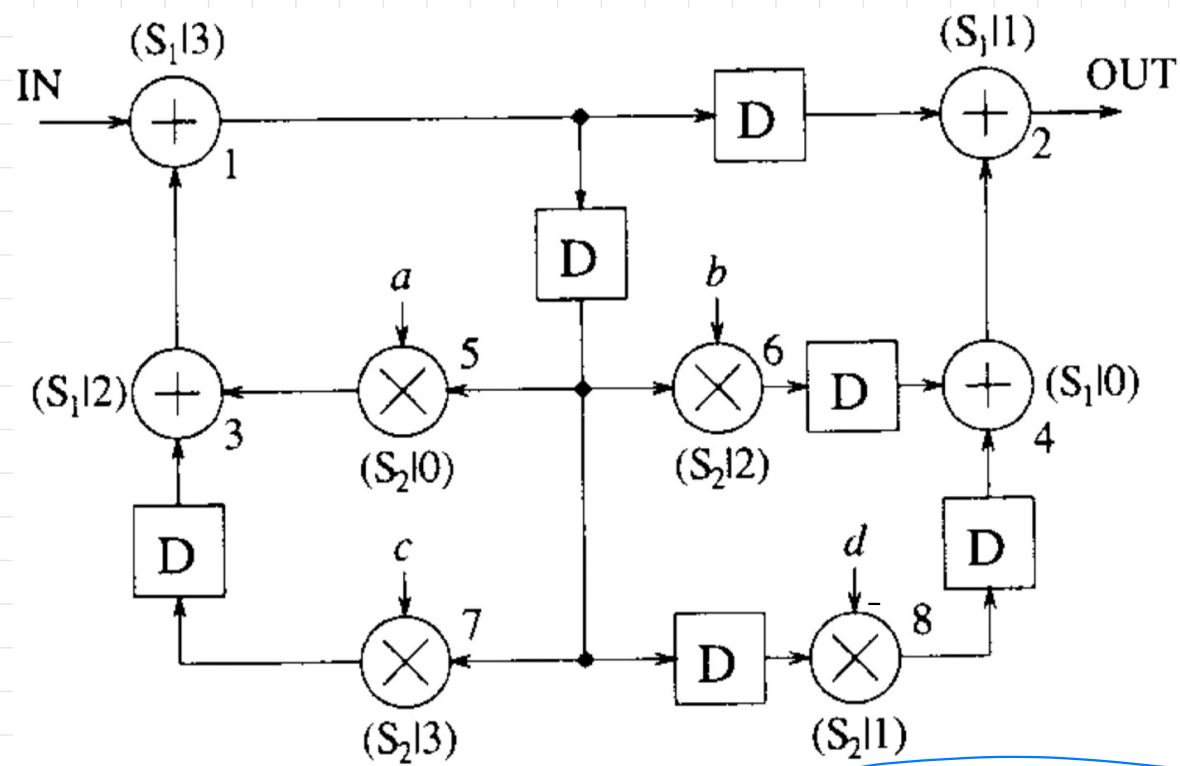


$$\begin{aligned}
 D_F(1 \rightarrow 2) &= 4(1) - 1 + 1 - 3 = 1 \\
 D_F(1 \rightarrow 5) &= 4(1) - 1 + 0 - 3 = 0 \\
 D_F(1 \rightarrow 6) &= 4(1) - 1 + 2 - 3 = 2 \\
 D_F(1 \rightarrow 7) &= 4(1) - 1 + 3 - 3 = 3 \\
 D_F(1 \rightarrow 8) &= 4(2) - 1 + 1 - 3 = 5 \\
 D_F(3 \rightarrow 1) &= 4(0) - 1 + 3 - 2 = 0 \\
 D_F(4 \rightarrow 2) &= 4(0) - 1 + 1 - 0 = 0 \\
 D_F(5 \rightarrow 3) &= 4(0) - 2 + 2 - 0 = 0 \\
 D_F(6 \rightarrow 4) &= 4(1) - 2 + 0 - 2 = 0 \\
 D_F(7 \rightarrow 3) &= 4(1) - 2 + 2 - 3 = 1 \\
 D_F(8 \rightarrow 4) &= 4(1) - 2 + 0 - 1 = 1.
 \end{aligned}$$

 




Folding Transform

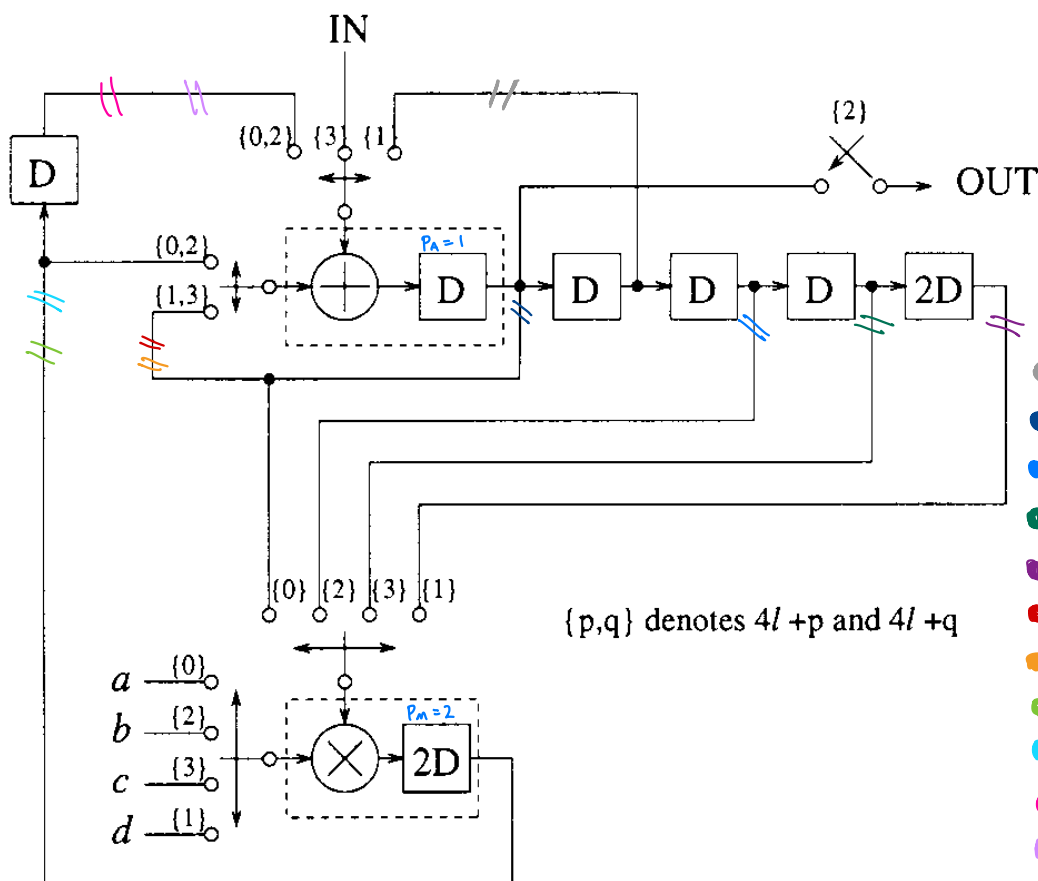

$\{p, q\}$ denotes $4l + p$ and $4l + q$

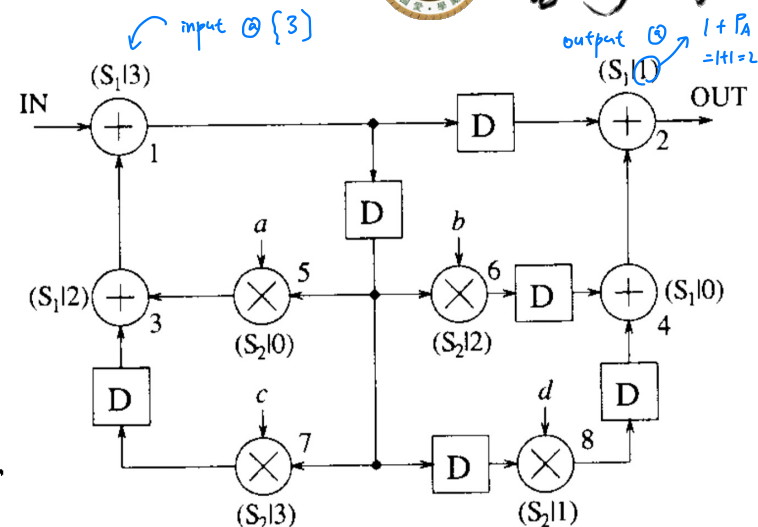

- $D_F(1 \rightarrow 2) = 4(1) - 1 + 1 - 3 = 1$
- $D_F(1 \rightarrow 5) = 4(1) - 1 + 0 - 3 = 0$
- $D_F(1 \rightarrow 6) = 4(1) - 1 + 2 - 3 = 2$
- $D_F(1 \rightarrow 7) = 4(1) - 1 + 3 - 3 = 3$
- $D_F(1 \rightarrow 8) = 4(2) - 1 + 1 - 3 = 5$
- $D_F(3 \rightarrow 1) = 4(0) - 1 + 3 - 2 = 0$
- $D_F(4 \rightarrow 2) = 4(0) - 1 + 1 - 0 = 0$
- $D_F(5 \rightarrow 3) = 4(0) - 2 + 2 - 0 = 0$
- $D_F(6 \rightarrow 4) = 4(1) - 2 + 0 - 2 = 0$
- $D_F(7 \rightarrow 3) = 4(1) - 2 + 2 - 3 = 1$
- $D_F(8 \rightarrow 4) = 4(1) - 2 + 0 - 1 = 1$



Retiming for Folding (1/6)

- Realizable folding: $D_F(U \xrightarrow{e} V) \geq 0$
- Once valid folding sets have been assigned, retiming can be used to either satisfy this property or determine that the folding sets are not feasible

Retiming for Folding (2/6)

■ Retiming constraints:

$$w_r(e) = w(e) + r(V) - r(U),$$

$$D'_F(U \xrightarrow{e} V) \geq 0$$

$$Nw_r(e) - P_U + v - u \geq 0.$$


$$N(w(e) + r(V) - r(U)) - P_U + v - u \geq 0.$$

$$r(U) - r(V) \leq \frac{D_F(U \xrightarrow{e} V)}{N}.$$

$$r(U) - r(V) \leq \left\lfloor \frac{D_F(U \xrightarrow{e} V)}{N} \right\rfloor$$



Retiming for Folding (3/6)

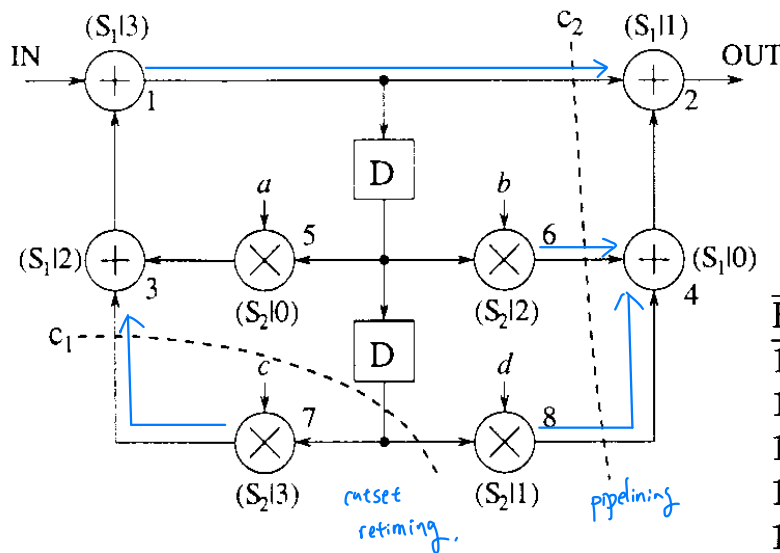

$$r(U) - r(V) \leq \left\lfloor \frac{D_F(U \xrightarrow{e} V)}{N} \right\rfloor$$


Edge	Folding Equation	Retiming for Folding Constraint
1 → 2	$D_F(1 \rightarrow 2) = -3$	$r(1) - r(2) \leq -1$ ✓
1 → 5	$D_F(1 \rightarrow 5) = 0$	$r(1) - r(5) \leq 0$
1 → 6	$D_F(1 \rightarrow 6) = 2$	$r(1) - r(6) \leq 0$
1 → 7	$D_F(1 \rightarrow 7) = 7$	$r(1) - r(7) \leq 1$
1 → 8	$D_F(1 \rightarrow 8) = 5$	$r(1) - r(8) \leq 1$
3 → 1	$D_F(3 \rightarrow 1) = 0$	$r(3) - r(1) \leq 0$
4 → 2	$D_F(4 \rightarrow 2) = 0$	$r(4) - r(2) \leq 0$
5 → 3	$D_F(5 \rightarrow 3) = 0$	$r(5) - r(3) \leq 0$
6 → 4	$D_F(6 \rightarrow 4) = -4$	$r(6) - r(4) \leq -1$ ✓
7 → 3	$D_F(7 \rightarrow 3) = -3$	$r(7) - r(3) \leq -1$ ✓
8 → 4	$D_F(8 \rightarrow 4) = -3$	$r(8) - r(4) \leq -1$ ✓

< 0 : too less delay elements


Retiming for Folding (4/6)

■ Constraint graph

 
- ☐ $r(1)=-1$
- ☐ $r(2)=0$
- ☐ $r(3)=-1$
- ☐ $r(4)=0$
- ☐ $r(5)=-1$
- ☐ $r(6)=-1$
- ☐ $r(7)=-2$
- ☐ $r(8)=-1$




Retiming for Folding (5/6)

 


Retiming

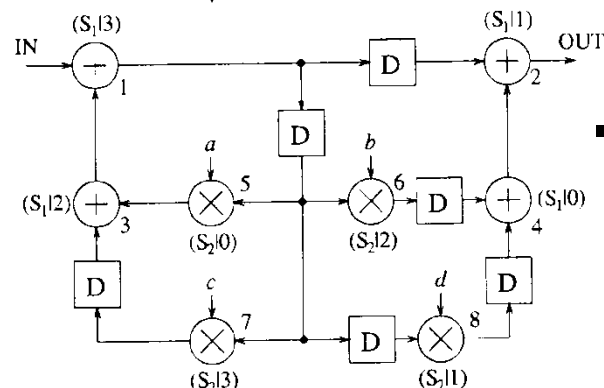


Folding

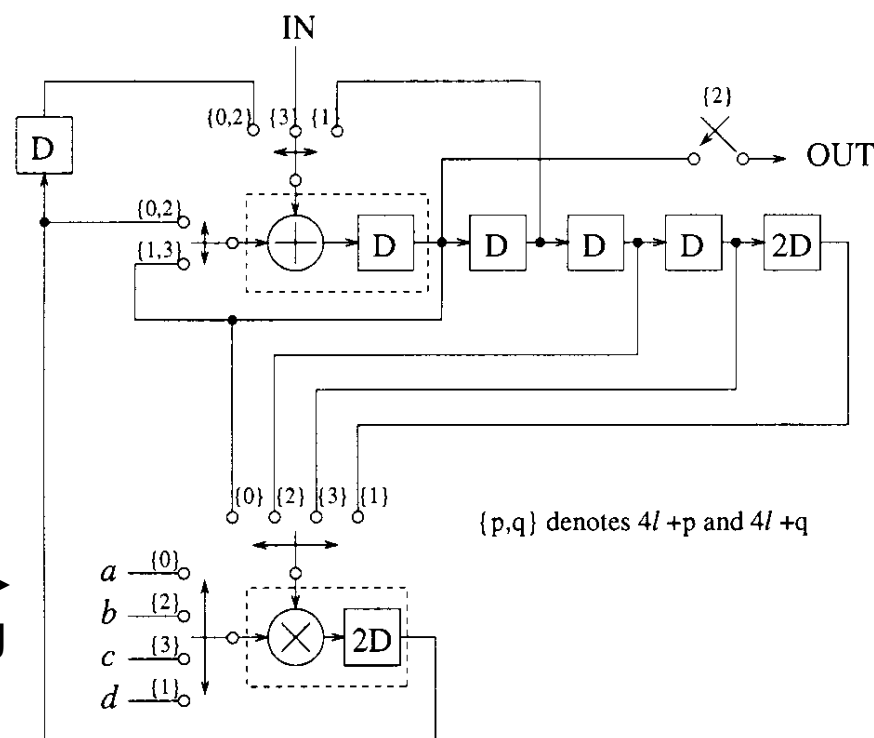

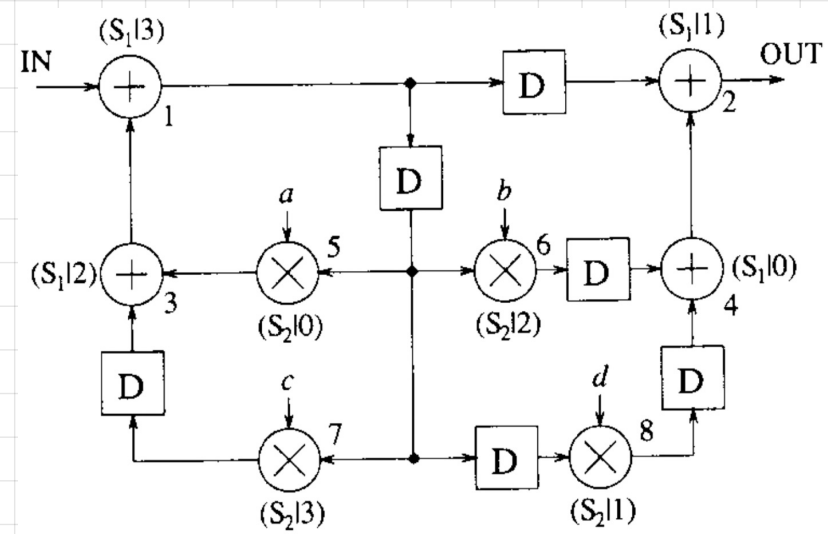


$$\begin{aligned}
 D_F(1 \rightarrow 2) &= 4(1) - 1 + 1 - 3 = 1 \\
 D_F(1 \rightarrow 5) &= 4(1) - 1 + 0 - 3 = 0 \\
 D_F(1 \rightarrow 6) &= 4(1) - 1 + 2 - 3 = 2 \\
 D_F(1 \rightarrow 7) &= 4(1) - 1 + 3 - 3 = 3 \\
 D_F(1 \rightarrow 8) &= 4(2) - 1 + 1 - 3 = 5 \\
 D_F(3 \rightarrow 1) &= 4(0) - 1 + 3 - 2 = 0 \\
 D_F(4 \rightarrow 2) &= 4(0) - 1 + 1 - 0 = 0 \\
 D_F(5 \rightarrow 3) &= 4(0) - 2 + 2 - 0 = 0 \\
 D_F(6 \rightarrow 4) &= 4(1) - 2 + 0 - 2 = 0 \\
 D_F(7 \rightarrow 3) &= 4(1) - 2 + 2 - 3 = 1 \\
 D_F(8 \rightarrow 4) &= 4(1) - 2 + 0 - 1 = 1.
 \end{aligned}$$

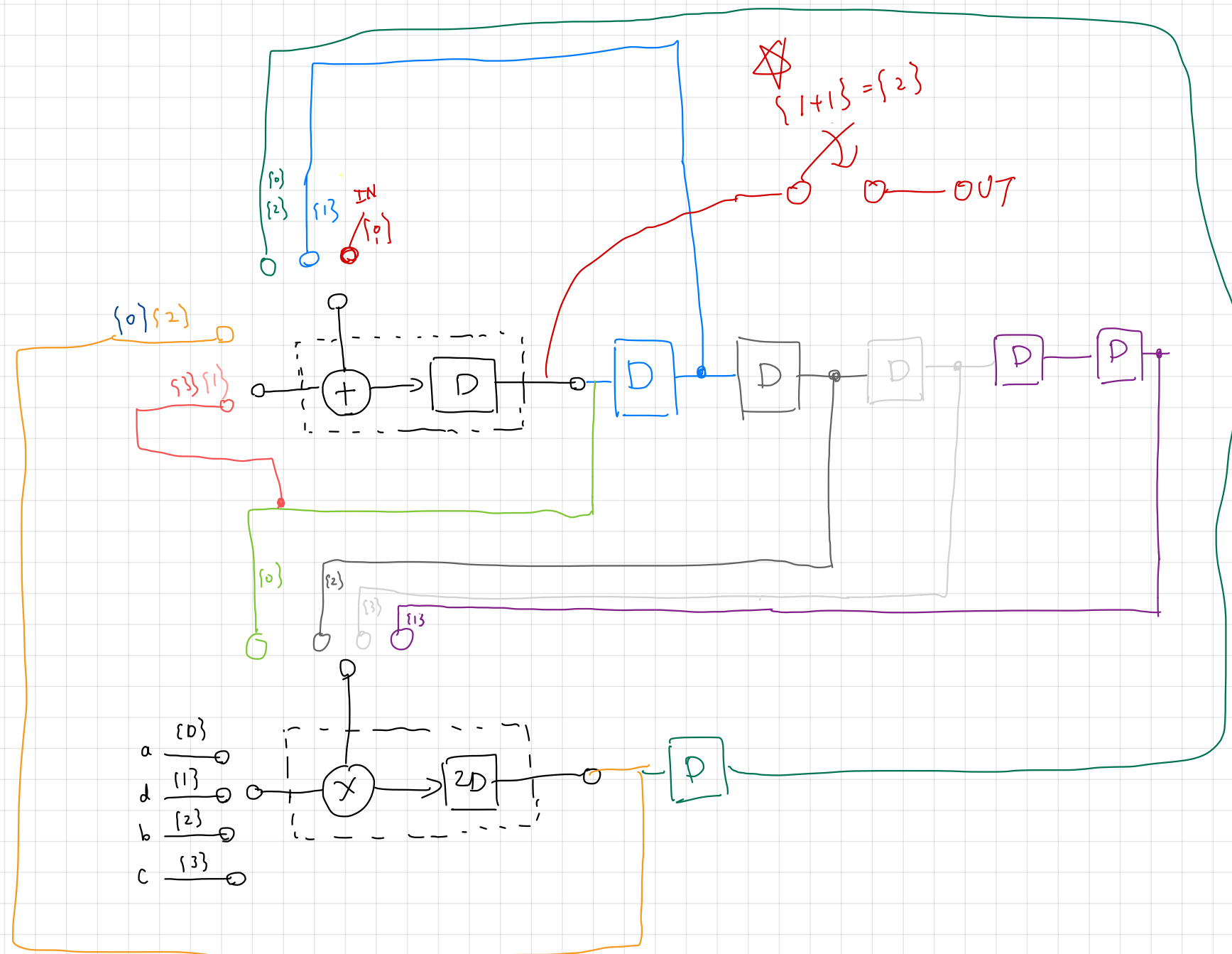

Retiming for Folding (6/6)

■ Another point of view

 - Apply cutset retiming at c_1 and c_2 to add/subtract w delays
- \rightarrow add/subtract Nw on D_F
- To make $D_F \geq 0$



Edge	Folding Equation	Retiming for Folding Constraint
$1 \rightarrow 2$	$D_F(1 \rightarrow 2) = -3$	$r(1) - r(2) \leq -1$
$1 \rightarrow 5$	$D_F(1 \rightarrow 5) = 0$	$r(1) - r(5) \leq 0$
$1 \rightarrow 6$	$D_F(1 \rightarrow 6) = 2$	$r(1) - r(6) \leq 0$
$1 \rightarrow 7$	$D_F(1 \rightarrow 7) = 7$	$r(1) - r(7) \leq 1$
$1 \rightarrow 8$	$D_F(1 \rightarrow 8) = 5$	$r(1) - r(8) \leq 1$
$3 \rightarrow 1$	$D_F(3 \rightarrow 1) = 0$	$r(3) - r(1) \leq 0$
$4 \rightarrow 2$	$D_F(4 \rightarrow 2) = 0$	$r(4) - r(2) \leq 0$
$5 \rightarrow 3$	$D_F(5 \rightarrow 3) = 0$	$r(5) - r(3) \leq 0$
$6 \rightarrow 4$	$D_F(6 \rightarrow 4) = -4$	$r(6) - r(4) \leq -1$
$7 \rightarrow 3$	$D_F(7 \rightarrow 3) = -3$	$r(7) - r(3) \leq -1$
$8 \rightarrow 4$	$D_F(8 \rightarrow 4) = -3$	$r(8) - r(4) \leq -1$

Register Minimization Techniques (1/8)




■ Lifetime analysis



- A procedure used to compute the minimum number of registers required to implement a DSP algorithm in hardware
- Ex:
 - a lives during time unit {1, 2, 3, 4}
 - b lives during time unit {2, 3, 4, 5, 6, 7}
 - c lives during time unit {5, 6, 7}

Register Minimization Techniques (2/8)

 ■ Lifetime analysis—linear lifetime chart



Minimum number of required registers

  


3 iterations with period N=6


Register Minimization Techniques (3/8)

- Lifetime analysis—lifetime table
- Ex: transpose matrix

 A Naive Way (Timing may not be correct): Shift Registers



Double Buffer (Pin-Pong buffer)

 

abc def ghi

↓
A⁻¹
↓
a d g b e h c f i

$$\begin{bmatrix} a & b & c \\ d & e & f \\ g & h & i \end{bmatrix}$$


Input in Raster Scan Order

$$T_{\text{output}} = T_{\text{zrlout}} + \text{latency}$$


Sample	T_{input}	T_{zrlout}	T_{diff}	T_{output}	Life Period ($T_{\text{input}} \rightarrow T_{\text{output}}$)
a	0	0	0	4	0 → 4
b	1	3	2	7	1 → 7
c	2	6	4	10	2 → 10
d	3	1	-2	5	3 → 5
e	4	4	0	8	4 → 8
f	5	7	2	11	5 → 11
g	6	2	-4	6	6 → 6
h	7	5	-2	9	7 → 9
i	8	8	0	12	8 → 12

Illegal! → add latency 4


Register Minimization Techniques (4/8)

 

Linear lifetime chart

 


Circular lifetime chart

 

cycle	i/p	p1	p2	p3	p4	o/p
0	a					
1	b	a				
2	c	b	a			
3	d	c	b	a		
4	e	d	c	b	a	a
5	f	e	d	c	b	d
6	a	f	e	d	c	g
7	h	c	f	e	d	b
8	i	h	c	f	e	e
9	x	i	h	c	f	h
10	x	x	i	h	c	c
11	x	x	x	i	h	f
12	x	x	x	x	i	i

Register Minimization Techniques (5/8)

 ■ Data allocation using forward-backward register allocation




N=9
Hashing

cycle	input	R1	R2	R3	R4	output
0	a					
1	b	a				
2	c	b	a			
3	d	c	b	a		
4	e	d	c	b	(a)	a
5	f	e	(d)	c	b	d
6	(g)	f	e		c	g
7	h		f	e		
8	i	h		f	(e)	e
9		i	(h)		f	h
10			i			
11				i		
12					(i)	i

cycle	input	R1	R2	R3	R4	output
0	a					
1	b	a				
2	c	b	a			
3	d	c	b	a		
4	e	d	c	b	(a)	a
5	f	e	(d)	c	(b)	d
6	(g)	f	e	(b)	(c)	g
7	h	(c)	f	e	(b)	(b)
8	i	h	(c)	f	(e)	e
9		i	(h)	(c)	(f)	h
10			i	(f)	(c)	(c)
11				i	(f)	(f)
12					(i)	i


Register Minimization Techniques (6/8)

cycle	input	R1	R2	R3	R4	output
0	a					
1	b	a				
2	c	b	a			
3	d	c	b	a		
4	e	d	c	b	a	a
5	f	e	d	c	b	d
6	g	f	e	b	c	g
7	h	c	f	e	b	b
8	i	h	c	f	e	e
9		i	h	c	f	h
10			i	f	c	c
11				i	f	f
12					i	i

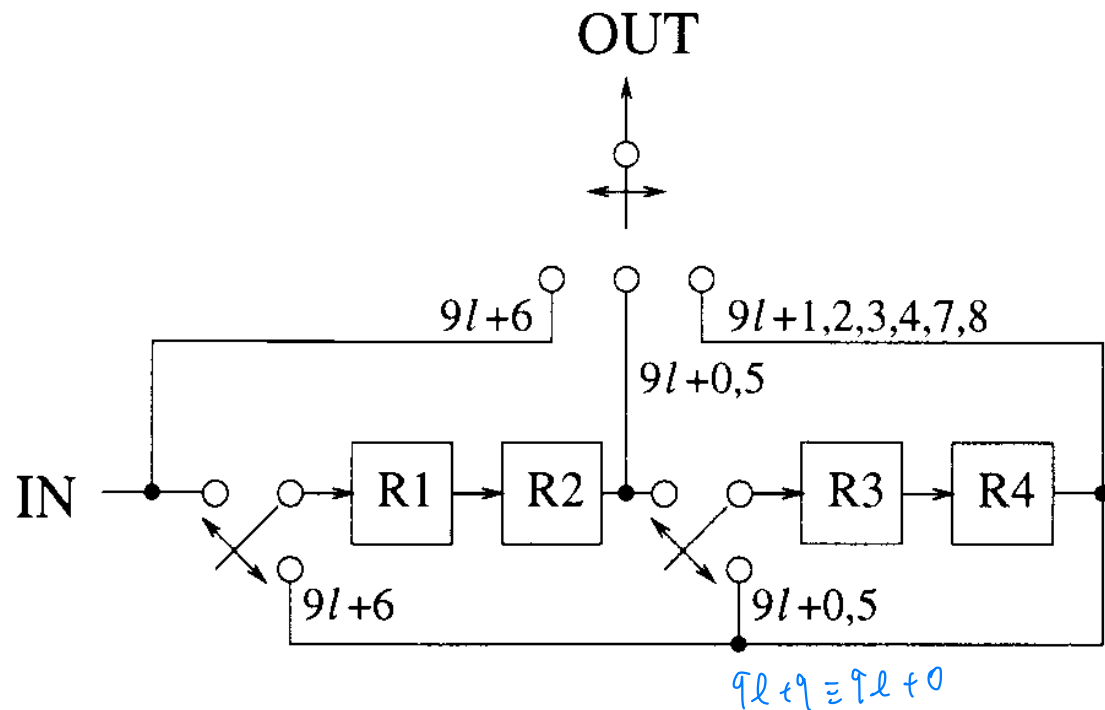



Register Minimization Techniques (7/8)

 


cycle	input	R1	R2	R3	output
0	a				
1	b	a			
2		b	a		
3			b	a	
4	c			b	
5				c	
6				c	
7				c	c

cycle	input	R1	R2	R3	output
0	a				
1	b	a			
2		b	a		
3			b	a	
4	c		(a)	b	a
5			b		
6			c	b	
7			(b)	(c)	b,c

Register Minimization Techniques (8/8)

cycle	input	R1	R2	R3	output
0	a				
1	b	a			
2		b	a		
3			b	a	
4	c		(a)	b	a
5		c	b		
6			c	b	
7			(b)	(c)	b,c

 



Register Minimization in Folded Architecture (1/4)



- Perform retiming for folding
- Write the folding equations
- Use the folding equations to construct a lifetime table
- Draw the lifetime chart and determine the required number of registers
- Perform forward-backward register allocation
- Draw the folded architecture that uses the minimum number of registers

Register Minimization in Folded Architecture (2/4)

■ Lifetime table

□ T_{input} of node U is $u + P_U$

  □ T_{output} of the node U is $u + P_U + \max_V \{D_F(U \rightarrow V)\}$




$$\begin{aligned}
 D_F(1 \rightarrow 2) &= 4(1) - 1 + 1 - 3 = 1 \\
 D_F(1 \rightarrow 5) &= 4(1) - 1 + 0 - 3 = 0 \\
 D_F(1 \rightarrow 6) &= 4(1) - 1 + 2 - 3 = 2 \\
 D_F(1 \rightarrow 7) &= 4(1) - 1 + 3 - 3 = 3 \\
 D_F(1 \rightarrow 8) &= 4(2) - 1 + 1 - 3 = 5 \\
 D_F(3 \rightarrow 1) &= 4(0) - 1 + 3 - 2 = 0 \\
 D_F(4 \rightarrow 2) &= 4(0) - 1 + 1 - 0 = 0 \\
 D_F(5 \rightarrow 3) &= 4(0) - 2 + 2 - 0 = 0 \\
 D_F(6 \rightarrow 4) &= 4(1) - 2 + 0 - 2 = 0 \\
 D_F(7 \rightarrow 3) &= 4(1) - 2 + 2 - 3 = 1 \\
 D_F(8 \rightarrow 4) &= 4(1) - 2 + 0 - 1 = 1
 \end{aligned}$$

node	$T_{\text{input}} \rightarrow T_{\text{output}}$
1	4 → 9
2	—
3	3 → 3
4	1 → 1
5	2 → 2
6	4 → 4
7	5 → 6
8	3 → 4

$(S_1|3) + \text{adder} = 3 + 1 = 4$

$(S_2|3) + \text{adder} = 3 + 2 = 5$

 Register Minimization in Folded Architecture (3/4)




cycle	input	R1	R2	output
0				
1				
2				
3	n_8			
4	n_1	(n_8)		n_8
5	n_7	n_1		
6		(n_7)	n_1	n_7
7			n_1	
8			n_1	
9			(n_1)	n_1


Register Minimization in Folded Architecture (4/4)

■ Number of registers: 6 → 2

cycle	input	R1	R2	output
0				
1				
2				
3	n_8			
4	n_1	(n_8)		n_8
5	n_7	n_1		
6		(n_7)	n_1	n_7
7			n_1	
8			(n_1)	
9			n_1	

 


$\{p,q\}$ denotes $4l+p$ and $4l+q$

 

$$\begin{aligned}
 D_F(1 \rightarrow 2) &= 4(1) - 1 + 1 - 3 = 1 \\
 D_F(1 \rightarrow 5) &= 4(1) - 1 + 0 - 3 = 0 \\
 D_F(1 \rightarrow 6) &= 4(1) - 1 + 2 - 3 = 2 \\
 D_F(1 \rightarrow 7) &= 4(1) - 1 + 3 - 3 = 3 \\
 D_F(1 \rightarrow 8) &= 4(2) - 1 + 1 - 3 = 5 \\
 D_F(3 \rightarrow 1) &= 4(0) - 1 + 3 - 2 = 0 \\
 D_F(4 \rightarrow 2) &= 4(0) - 1 + 1 - 0 = 0 \\
 D_F(5 \rightarrow 3) &= 4(0) - 2 + 2 - 0 = 0 \\
 D_F(6 \rightarrow 4) &= 4(1) - 2 + 0 - 2 = 0 \\
 D_F(7 \rightarrow 3) &= 4(1) - 2 + 3 - 2 = 1 \\
 D_F(8 \rightarrow 4) &= 4(1) - 2 + 0 - 1 = 1.
 \end{aligned}$$

cycle	input	R1	R2	output
0				
1				
2				
3	n_8			
4	n_1	(n_8)		n_8
5	n_7	(n_1)		
6		(n_7)	n_1	n_7
7			n_1	
8			n_1	
9			(n_1)	n_1

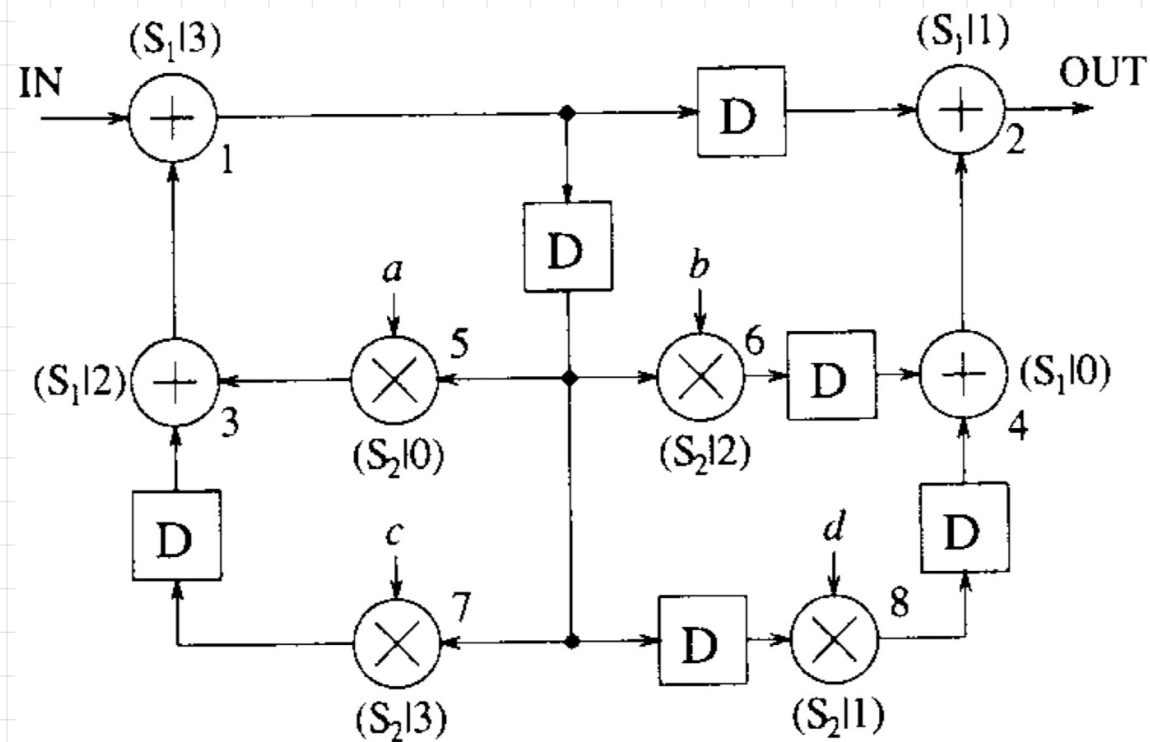

$$\begin{aligned}
 D_F(1 \rightarrow 2) &= 4(1) - 1 + 1 - 3 = 1 \\
 D_F(1 \rightarrow 5) &= 4(1) - 1 + 0 - 3 = 0 \\
 D_F(1 \rightarrow 6) &= 4(1) - 1 + 2 - 3 = 2 \\
 D_F(1 \rightarrow 7) &= 4(1) - 1 + 3 - 3 = 3 \\
 D_F(1 \rightarrow 8) &= 4(2) - 1 + 1 - 3 = 5 \\
 D_F(3 \rightarrow 1) &= 4(0) - 1 + 3 - 2 = 0 \\
 D_F(4 \rightarrow 2) &= 4(0) - 1 + 1 - 0 = 0 \\
 D_F(5 \rightarrow 3) &= 4(0) - 2 + 2 - 0 = 0 \\
 D_F(6 \rightarrow 4) &= 4(1) - 2 + 0 - 2 = 0 \\
 D_F(7 \rightarrow 3) &= 4(1) - 2 + 2 - 3 = 1 \\
 D_F(8 \rightarrow 4) &= 4(1) - 2 + 0 - 1 = 1
 \end{aligned}$$

